

Mini Project 3
Nusair Islam
37373826


Table of Contents

Part 1.....	3
A.....	3
B.....	5
C.....	7
D.....	8
 Part 2.....	 8
A.....	8
B.....	9
C.....	10
 Part 3.....	 8
A.....	11
B.....	14
C.....	14
 Part 4.....	 14
A.....	15
B.....	15
C.....	16

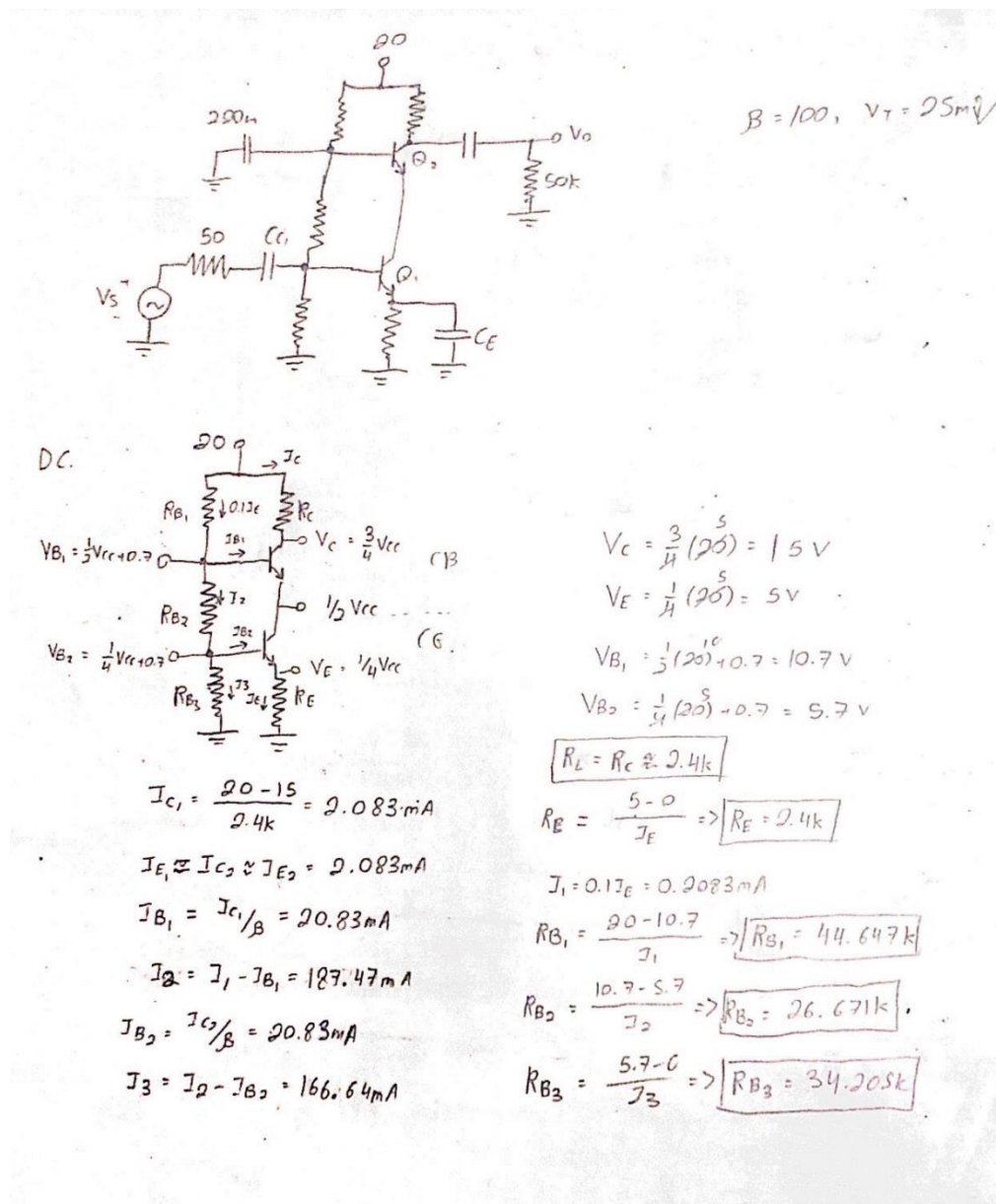Part 1

I found that the β for a 2N3904 transistor ranges between 100-300, I will set $\beta = 300$ for my calculations for both transistors.

I used the $1/4^{\text{th}}$ rule to figure out the resistor values, at DC analysis, the capacitors act like open circuits. I witnessed in MP2 that the load resistance is equivalent to R_c , so I set R_c to be around 2.5k since that is the required R_{out} , and the closest common resistor value is 2.4k, therefore, $R_c = 2.4k\Omega$.



DC Operating points

$$I_{B1} = 7.429\mu A$$

$$I_{C1} = 2.289mA$$

$$I_{E1} = -2.296mA$$

$$V_{BE1} = 0.676V \quad V_{CE1} = 3.94V$$

$$I_{b2} = 7.375 \mu A$$

$$I_{c2} = 2.296 mA$$

$$I_{e2} = 2.304 mA$$

$$V_{be2} = 0.676 V \quad V_{ce2} = 5.035 V$$

Now that I have a value for I_c , I will use these values to find g_m and r_{π} . I assumed $V_T = 25 mV$

$$g_{m1} = I_{c1}/V_T = 91.56 mS \quad r_{\pi1} = \beta/g_{m1} = 327.7 \Omega$$

$$g_{m2} = I_{c2}/V_T = 91.84 mS \quad r_{\pi2} = \beta/g_{m2} = 326.7 \Omega$$

This is my work to find capacitance values

Low f: C_B is huge so it shorts when you analyze other caps

$R_{BB} = R_{B2} \parallel R_{B3} = 14.986 k$

C_{C2} is independent from the rest of the circuit, so

$$\omega_{p_{C2}} = \frac{1}{(2.4k + 2.4k) C_{C2}}$$

C_{C1} will short before the other caps, do DC test on C_{C1}

$$I_{test} = \frac{V_1 - V_2}{R_{C1} + r_{\pi1} + R_{BB}}$$

$$R_{eq} = \frac{V_1 - V_2}{I_{test}} = 10.522 k$$

$$\omega_{p_{C1}} = \frac{1}{R_{eq} C_{C1}}$$

Do SC test on C_{C2}

$$\frac{V_1}{50} + \frac{V_1}{14.986k} + \frac{V_1 - 1}{327.7} = 0$$

$$91.56 mS \cdot (V_1 - 1) + \frac{V_1 - 1}{327.7} + I_{test} = \frac{1}{2.4k}$$

$$R_{eq2} = \frac{1}{I_{test}} = 10.12$$

$$\omega_{L_{FE}} = \frac{1}{10.12 \cdot C_E} > \omega_{L_{CE}} = \frac{1}{2.4k \cdot C_E}$$

C_E sees the smallest R , so it will have the dominant pole. Use that pole to find the C_E .

$$500:2\pi = \frac{1}{10.12 C_E} \rightarrow C_E = \frac{1}{10.12 \cdot 500 \cdot 2\pi} = 26.263 nF \rightarrow \text{closest cap} \rightarrow C_E = 22 nF$$



For economic sake I'll set $C_{C1} = C_{C2} = C_E = 22 nF$

CS Scanned with CamScanner


$$\omega_{LPMS} = \sqrt{\omega_{p1}^2 + \omega_{p2}^2 + \omega_{p3}^2} = 3.451 k rad/s \rightarrow f_{LPMS} = 546.88 Hz$$

B Compare ω_{L3dB} values

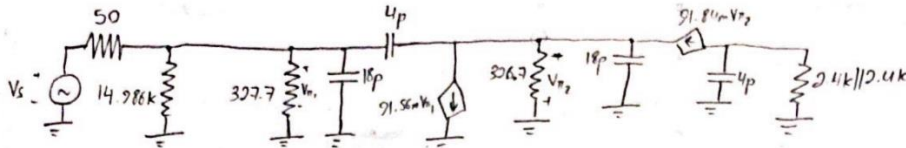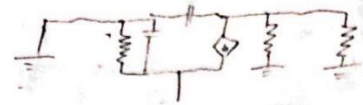High freq: From datasheet $C_\pi = 18pF$, $C_m = 4pF$



Get 3 circuits

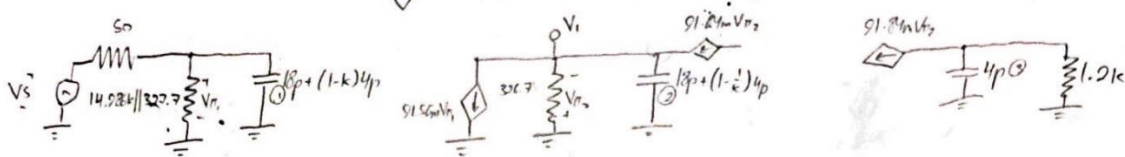

Get k : KCL around V_1

$$91.56mV_{\pi_1} + \frac{V_1}{326.7} = 91.84mV_{\pi_2}, \quad V_{\pi_2} = -V_1$$

$$91.56mV_{\pi_1} = -V_1 \left(\frac{1}{326.7} + 91.84m \right)$$

$$k = \frac{V_1}{V_{\pi}} = - \frac{91.56m}{91.84m} \approx -1$$

$$\omega_{HP1} = \left[(18p + 2(4p)) \cdot 50 \parallel 14.986k \parallel 327.7 \right]^{-1} = 8.822 \cdot 10^8 \text{ rad/s} = \omega_{HP1}$$


$$\omega_{HP3} = [4p \cdot 1.2k]^{-1} = 2.083 \cdot 10^9 \text{ rad/s} = \omega_{HP3}$$

$$\omega_{HP2} = \left[\frac{r_{\pi}}{14.9} (18p + 2(4p)) \right]^{-1} = 3.544 \cdot 10^{10} \text{ rad/s} = \omega_{HP2}$$

$$\omega_{HP3dB} = \sqrt{\frac{1}{\omega_{HP1}^2} + \frac{1}{\omega_{HP2}^2} + \frac{1}{\omega_{HP3}^2}}^{-1} = 2.028 \cdot 10^9 \text{ rad/s} = \omega_{HP3dB}$$

$$f_{LP3dB} = 3.228 \cdot 10^7 \text{ Hz}$$


This is my final circuit:

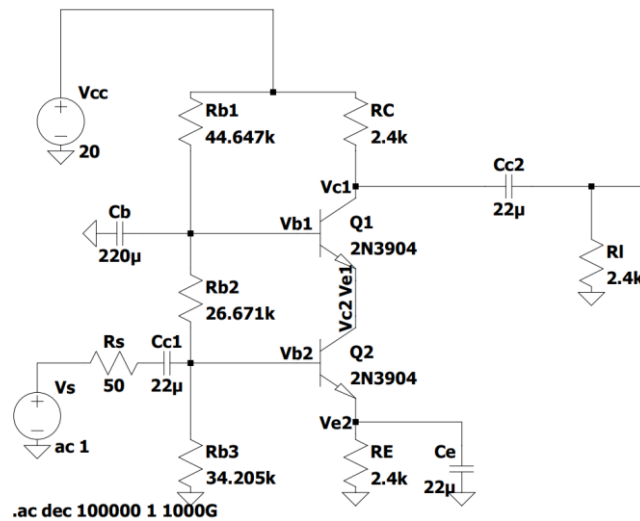

I calculated my ω_{Lp3dB} as 3.751k rad/s $\rightarrow f_{Lp3dB} = 596.88\text{Hz}$

I calculated my ω_{Hp3dB} as 202.8 Mrad/s $\rightarrow f_{Hp3dB} = 32.28\text{ MHz}$

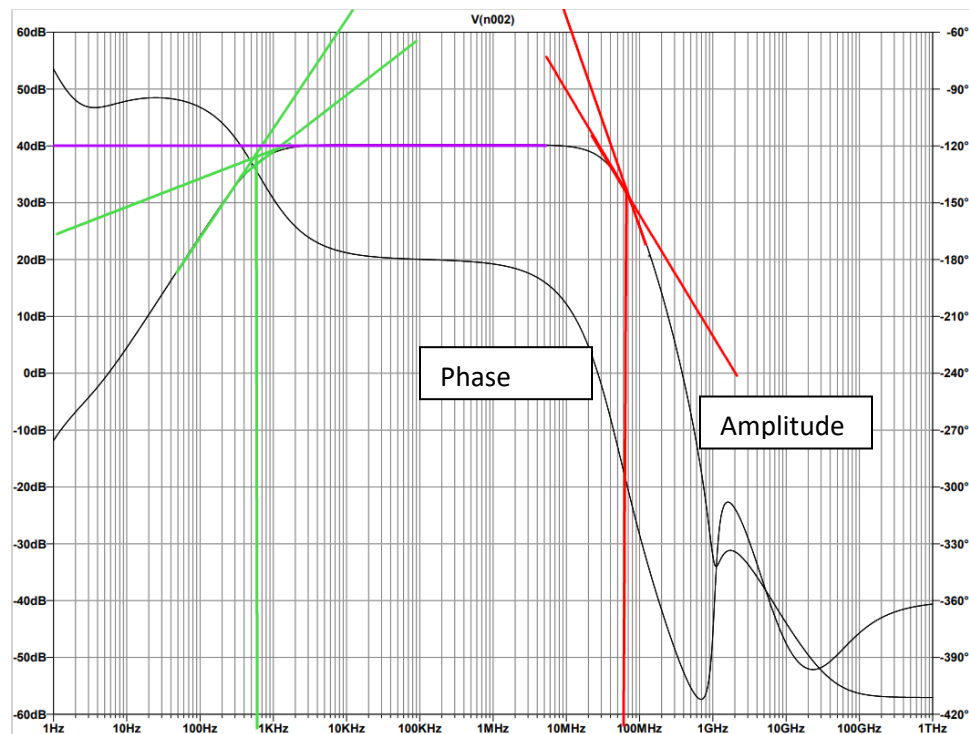
By taking the transfer function and using the linear approximation method shown below using Gimp: I get my $f_{Lp3dB} = \sim 600$ and $f_{Hp3dB} = \sim 45\text{M}$. These values do have a lot of error with the method I use, however.




	f_{Lp3dB}	f_{Hp3dB}
Calculated	596.88	32.28M
Simulated	600	45M
% Difference	0.52%	28.267%

C Use $f = 100\text{kHz}$ as midband frequency

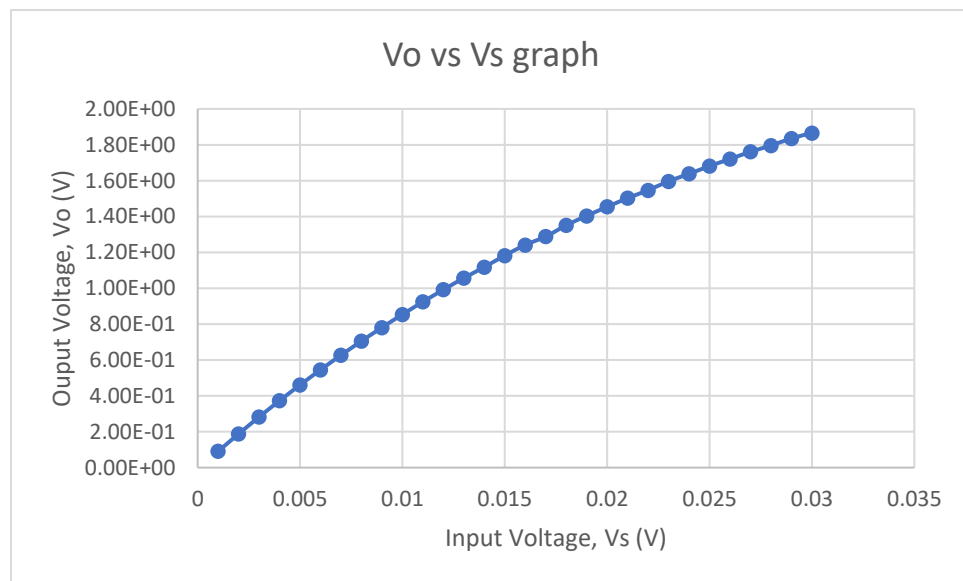I incremented the input voltage from 1mV to 30mV, I see that it stops being linear after around 15mV



The resulting midband graph is

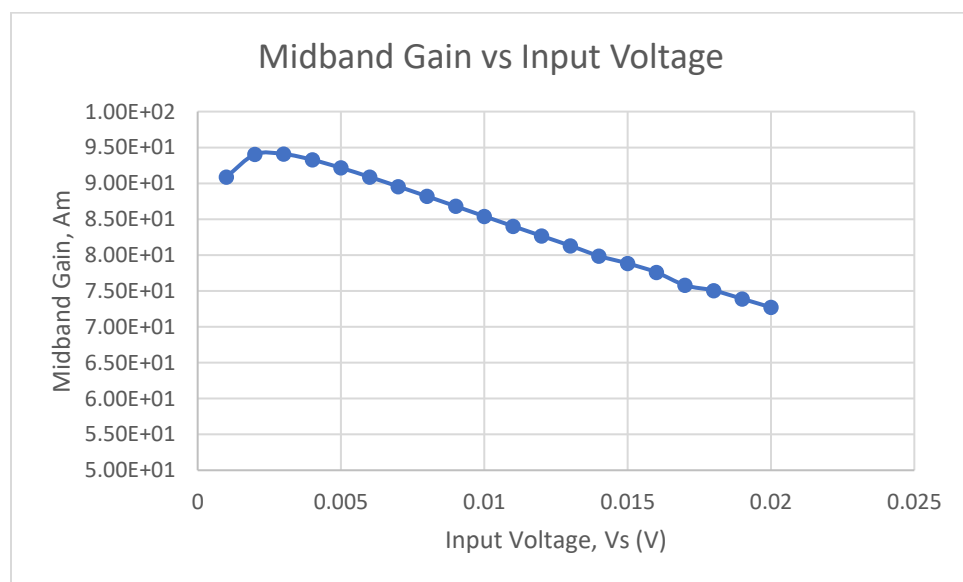

The linear portion of the input voltage is within our specification of $A_v > 50$ which is correct!

D

I took out the 50-ohm resistor, set my voltage amplitude to 10mV for 100kHz frequency, and measured input resistance to be: $R_{in} = 10\text{mV}/2.95\mu\text{A} = 4\text{k}$

$R_{out} = 0.9\text{V}/515\mu\text{A} = 1.748\text{k}$

Part 2

A Find resistor and capacitor values

DC:

Midband:

Redraw DC:

Handwritten calculations and notes:

$\beta = 300$

$V_T = \frac{kT}{q} \approx 26\text{mV}$

$i_B + i_C = i_E$

$\frac{V_{T1}}{r_{\pi 1}} + \frac{V_{T1} \cdot \beta}{r_{\pi 1}} = i_{E1} \Rightarrow \frac{V_{T1}}{r_{\pi 1}} (1 + \beta) = i_{E1} (1 + \beta)$

$R_{in} = \left(\frac{r_{\pi 1}}{1 + \beta} \right) \parallel R_{E1} = 50$

$= \frac{\beta}{g_{m1} (1 + \beta)} \parallel R_{E1} = 50$

$= \frac{\beta}{1 + \beta} \cdot \frac{V_T}{I_{E1}} \parallel R_{E1} = 50$

$= \frac{I_{E1}}{V_T} + \frac{1}{R_{E1}} = \frac{1}{50}$

$= I_{E1} \left(\frac{1}{V_T} + \frac{1}{R_{E1}} \right) = \frac{1}{50}$

$I_{E1} = I_{C1} = 0.5\text{mA}$

$R_{C1} = \frac{10 - 0.8}{I_{C1} + I_{B2}} = \frac{4}{I_{C1} + \frac{I_{C2}}{\beta}}$

$R_{C1} = 7.945\text{k}$

$V_{E1} = V_{BE} + V_E = 4.7$

$R_{B1} = \frac{10 - V_{B1}}{I_{B1}} = 148\text{k} = R_{B2}$

$I_{B1} = I_{C1} / \beta = 1.67\text{mA}$

$I_{C2} = I_{C1} - I_{B2} = 48.3\text{mA}$

$R_{B2} = \frac{V_{B2} - 0}{I_{B2}} = 97.241\text{k} = R_{B2}$

$R_{E1} = \frac{V_E}{I_{E1}} = \frac{1/3 (12)}{0.5\text{mA}} = 8\text{k} = R_{E1}$

$R_{out} = \left(\frac{R_{C1} + R_{E2}}{1 + \beta} \right) \parallel R_{E2} = 50$

$= \left(\frac{R_{C1}}{1 + \beta} + \frac{R_{E2}}{1 + \beta} \right) \parallel R_{E2}$

$= \left(\frac{R_{C1}}{1 + \beta} + \frac{\beta}{1 + \beta} \cdot \frac{1}{g_{m2}} \right) \parallel R_{E2} = \left(\frac{R_{C1}}{1 + \beta} + \frac{V_T}{I_{C2}} \right) \parallel R_{E2}$

$= \left(\frac{R_{C1}}{1 + \beta} + \frac{V_T \cdot R_{E2}}{I_{C2}} \right) \parallel R_{E2}$


$= \left(\frac{R_{C1}}{1 + \beta} + \frac{V_T \cdot R_{E2}}{I_{C2}} \right) \parallel R_{E2} = 50$

$R_{E2} = 6.998\text{k}$

Low freq:

$$g_{m1} = I_{C1}/V_T = 2.0 \cdot 10^{-2} = g_{m2} \quad r_{\pi1} = \beta/g_{m1} = 15k = r_{\pi2}$$

Assume Q_1 and Q_2 are the same

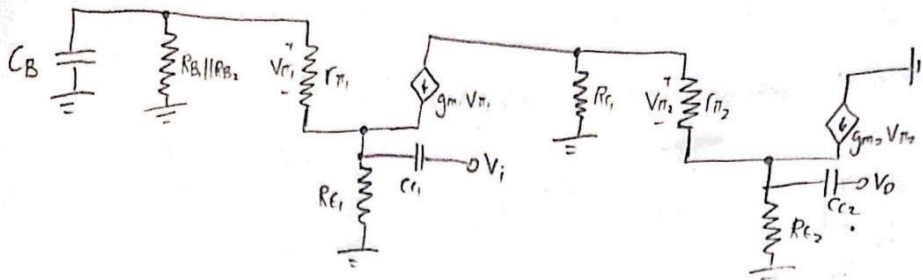

$$\omega_{LP2} = \left[\left(\frac{R_{C2} + r_{\pi2}}{1 + \beta} \parallel R_{E2} \right) \cdot C_{C2} \right]^{-1} = [75.408 \cdot C_{C2}]^{-1}$$

$$\text{SC around } C_{C1}: \omega_{LP1} = \left[\frac{r_{\pi1}}{1 + \beta} \parallel R_{E1} \cdot C_{C1} \right]^{-1} = [49.525 \cdot C_{C1}]^{-1}$$

$$C_{C1} \text{ and } C_{C2} \text{ set } \omega_{LP3dB} = 1000 \cdot 2\pi$$

$$C_{C2} = \frac{1}{75.408 \cdot 1000 \cdot 2\pi} = \boxed{2.11 \mu F}$$

$$C_{C1} = \frac{1}{49.525 \cdot 1000 \cdot 2\pi} = \boxed{3.214 \mu F}$$


C_B should have a very small pole contribution.

$$R_{C3} = R_B \parallel R_{B2} \parallel (r_{\pi1} + (1 + \beta) \cdot R_{E1}) = 5.699 \cdot 10^4$$

Let's say this cap is @ $\omega_{LPB} = 100$ (≈ 1 decade later)

$$C_B = \frac{1}{100 \cdot 5.699 \cdot 10^4} = \boxed{10.17546 \mu F = C_B}$$

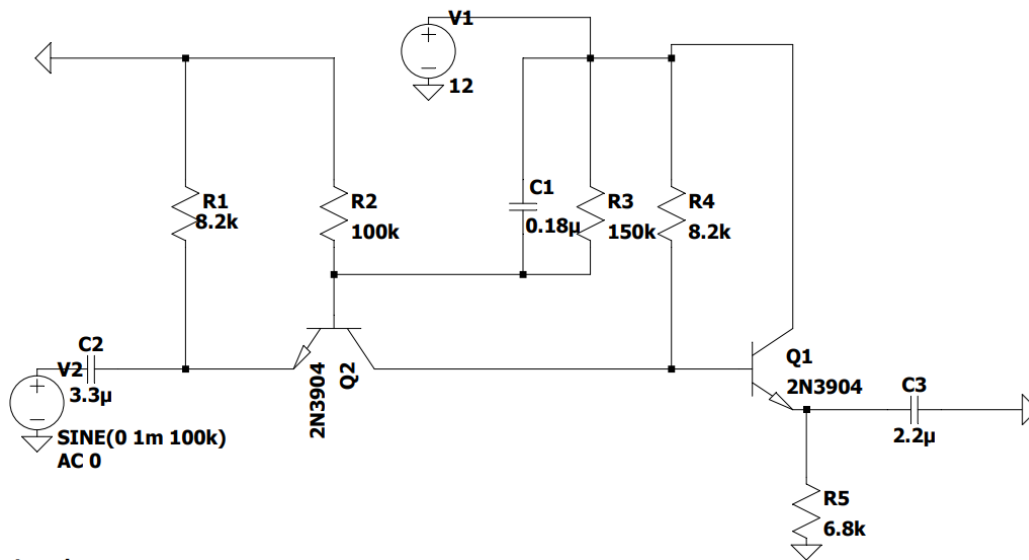B This is the circuit made using the resistance and capacitors values that were closest to the ones I calculated



I calculated R_{in} by attaching a voltage source to the input and measuring the peak voltage and peak current

$$R_{in} = V_{in_{pp}} / I_{in_{pp}} = 1\text{mV} / 20.029\mu\text{A} = \mathbf{49.434 \Omega = R_{in}}$$


I calculated R_o by attaching a voltage source to the input and measuring the peak voltage and peak current

$$R_o = V_{o_{pp}} / I_{o_{pp}} = 1\text{mV} / 20.15\mu\text{A} = \mathbf{49.628 \Omega = R_o}$$

I attached a source voltage of 1mV and left the load open to measure midband gain at 100kHz

$$A_m = V_o / V_s = 146.83\text{mV} / 1\text{mV} = \mathbf{146.83 = A_m}$$

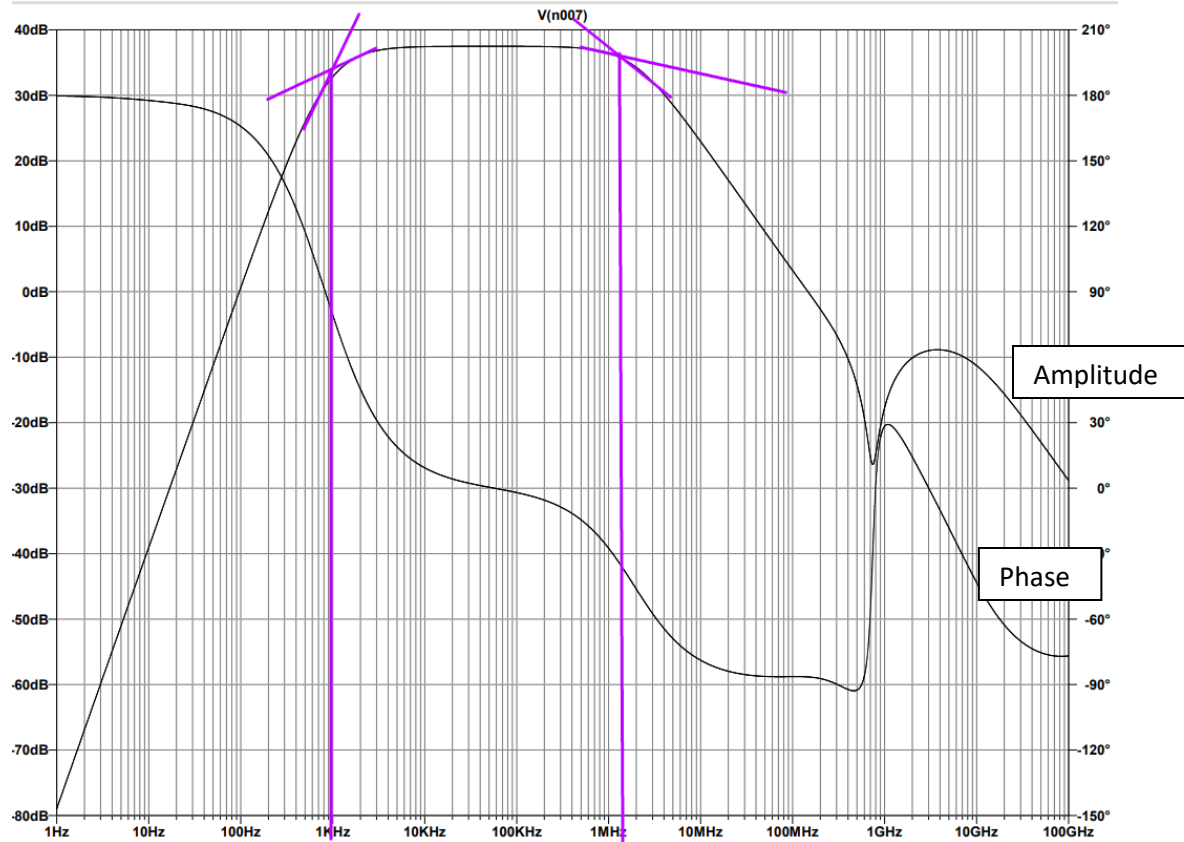C By loading the circuit I made, I resulted in the following bode plot




Based on the estimation of the bode plot I see that f_{Lp3dB} is located at around 1kHz which is what we wanted, and the f_{Hp3dB} is located at around 15MHz. Since the low-cutoff frequency matches what we wanted, our capacitor values must be correct!

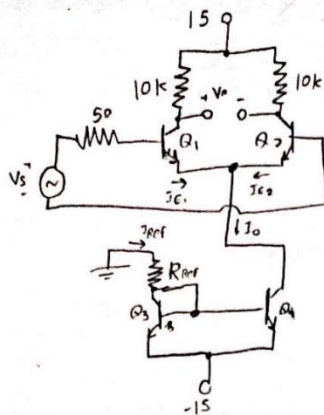Part 3

A Wire up circuit

This is how I found the required resistance values



$$\beta = 300$$

$$I_0 = I_{E1} + I_{C2} = 1mA + 1mA = 2mA$$

$$I_{Ref} = \frac{V - (V_{E1} + V_{BE})}{R_{Ref}} = I_{E3} + I_{B4}$$

$$I = I_{C2} = I_{E4} - I_{B4}$$

$$V_{BE3} = V_{BE4}$$


$$I_{E3} = I_{E4}$$

$$I_{Ref} = I_0 + 2I_{B2} = I_{C2} + 2I_{B2} = I_{C2} (1 + 2/\beta) = I_0 (1 + 2/\beta)$$



$$I_{Ref} = 2mA (1 + 2/\beta) = 2.013mA$$

$$R_{Ref} = \frac{V - (V_{EE} + V_{BE})}{I_{Ref}} = \frac{0 - (-15 + 0.7)}{2.013mA} = 7.103k$$

Low freq:

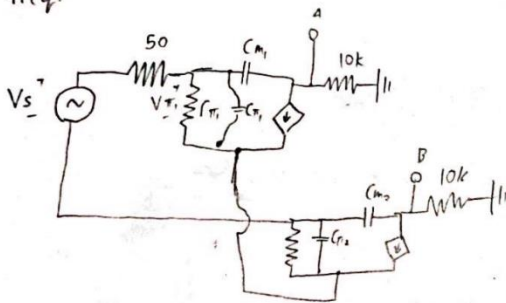

↓ Look nicer

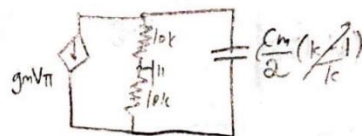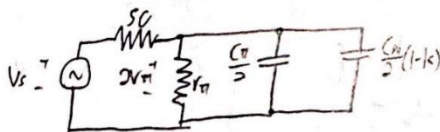

$$\frac{V_{\pi}}{V_s} = \frac{r_{\pi}}{2R_s + r_{\pi}} = 0.498 \quad \frac{V_o}{V_{\pi}} = -g_m \cdot (R_{C1} + R_{C2}) = -800$$

$$A_m = \frac{V_{\pi}}{V_s} \cdot \frac{V_o}{V_{\pi}} = 398.67$$

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = 40mS, \quad r_{\pi} = \frac{\beta}{g_m} = 7.5k, \quad C_{\pi} = 18p, \quad C_m = 4p$$

$$k = \frac{V_o}{V_{\pi}} \cdot \frac{1}{\beta} = 400$$


$$\omega_{HP1} = \left[\left(\frac{C_{\pi}}{2} + \frac{C_m}{2} (401) \right) \cdot (50 || 2r_{\pi}) \right]^{-1} = 2.474 \cdot 10^7 \text{ rad/s}$$

$$\omega_{HP2} = \left[\left(\frac{C_m}{2} (1 - \frac{1}{k}) \right) \cdot (10k + 10k) \right]^{-1} = 2.5 \cdot 10^7 \text{ rad/s}$$


$$\omega_{HP3dB} = \sqrt{\omega_{HP1}^2 + \omega_{HP2}^2} = 1.759 \cdot 10^7 \text{ rad/s} \rightarrow f_{HP3dB} = 2.796 \text{ MHz}$$

Scanned with CamScanner

This is my resultant circuit

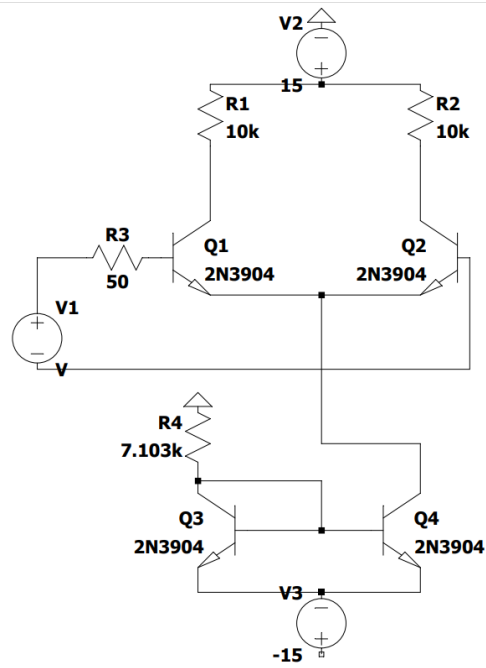

Here is the bode plot output

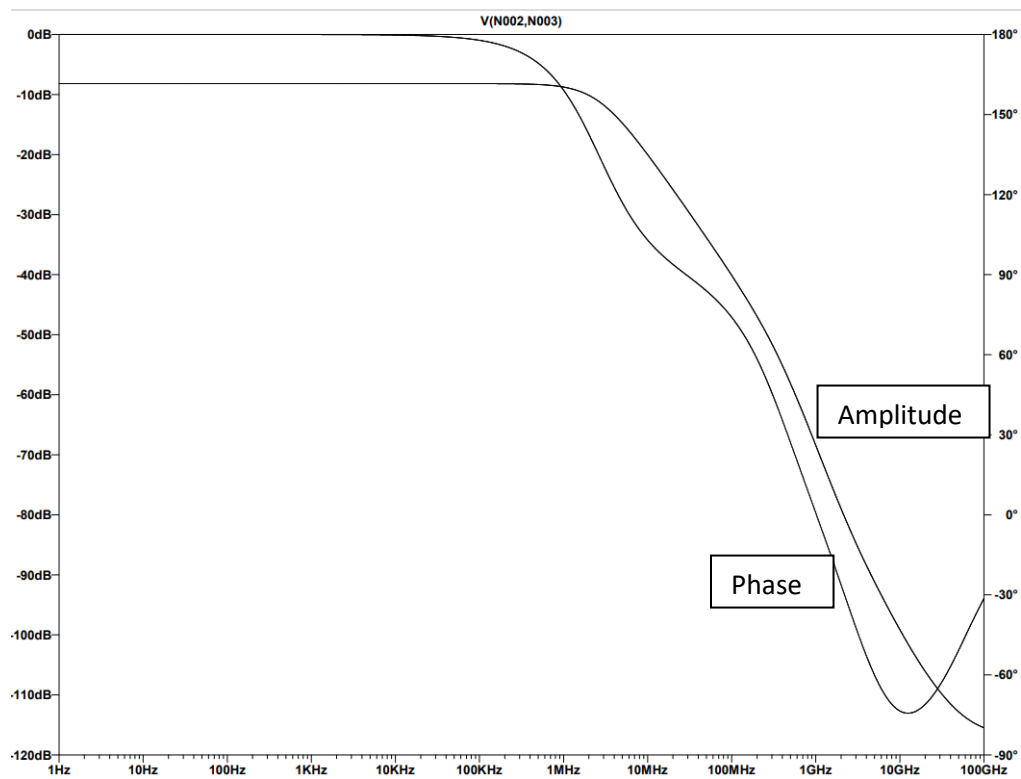


The f_{Hp3dB} is around 3.5MHz in this bode plot

B Find calculated poles

The calculated pole is $f_{Hp3dB} = 2.796\text{MHz}$. The % error is $\sim 20\%$. This error may be due to the approximation technique used to find the pole on the graph. Nevertheless, the poles were somewhat close

C I chose 10kHz as my midband frequency

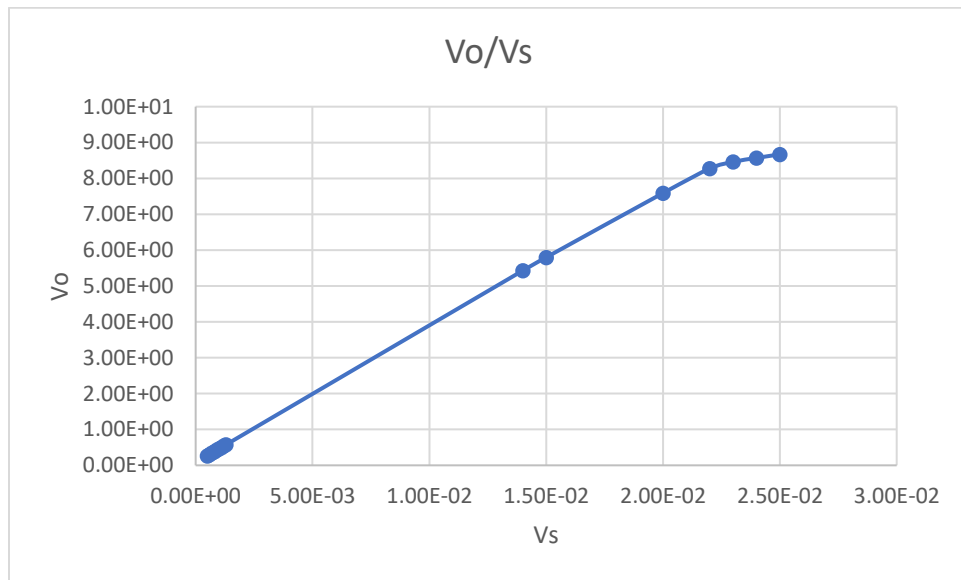
Increasing my voltage from 0.5mV to 25mV this is the graph I ended up with




As you can see, the graph stops getting linear at around 22mV, as well the midband gain during the linear portions was around 500 – 350 which fit with the midband gain I calculated as 400.

Part 4

Here is my circuit “wired up”

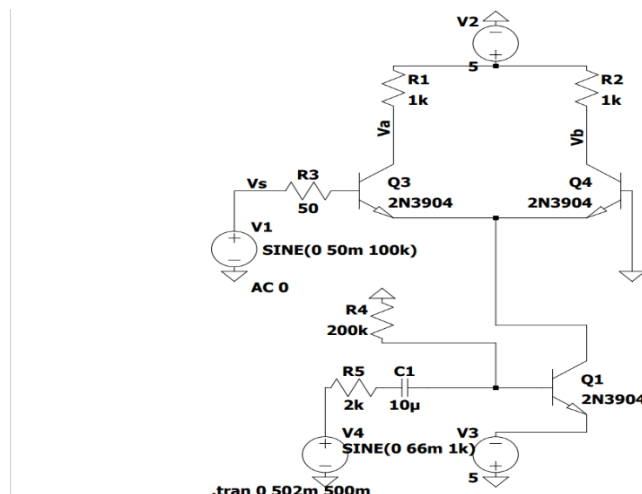

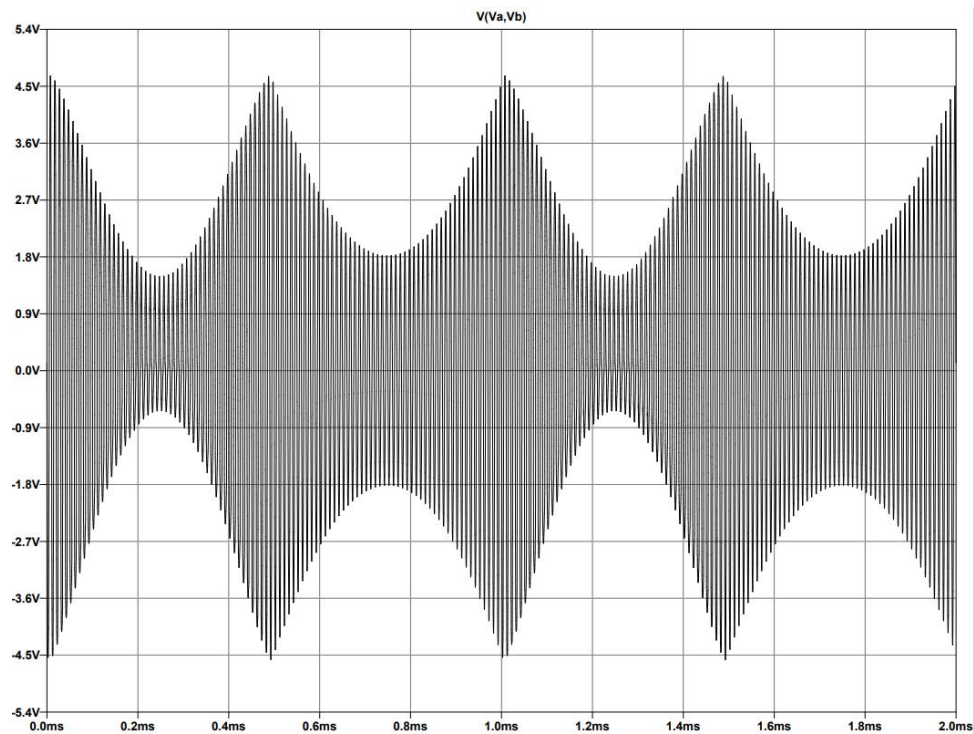
A Apply a 50m, 1kHz sine wave to input of modulator



The output appears to behave like “wave packets”, it looks like waves made of waves

B Vary amplitude of input signal (between 10m and 100mVp) and show what happens.

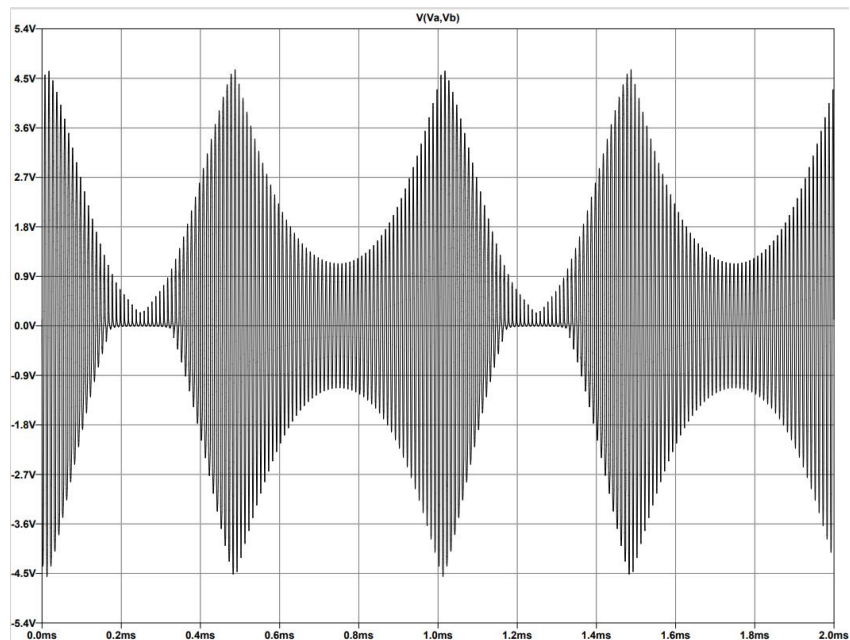
As the amplitude increases, the troughs of the wave packets get smaller as the peaks grow. At around 67 mV the wave packets appear to clip



Observe at the bottoms it starts flattening out

C Change input to a square wave

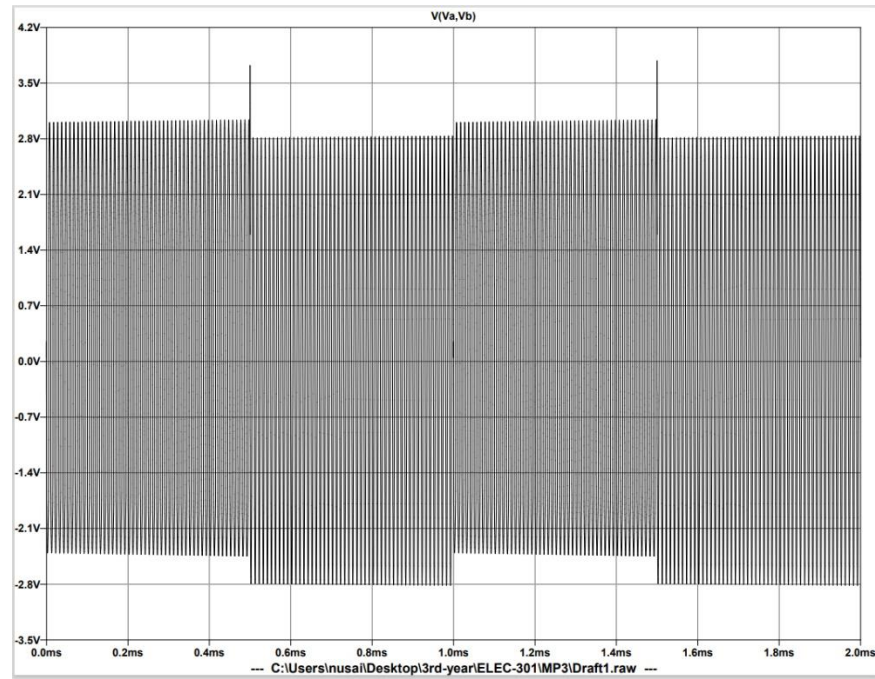The square wave causes the output to also become squared.



At around 60mV of amplitude, the signal starts getting a bit of noise, and a slight slope is visible as well as a large outlier point on every other wave. At around this amplitude, the signal starts distorting.

The AM modulator works because the two waves from the input are multiplied together and the resultant waveform is the amplitude modulation. This exercise helped me learn how they work, as well as limits which is kind of cool considering this is how old AM hobby radios are made